

# 1

Element	Calculated/Nominal Values	Measure Values	Percent Differences
$R_1$	$1.5K\Omega$	$1.475K\Omega$	-1.6666%
$R_2$	$3.3K\Omega$	$3.345K\Omega$	1.3636%
$R_3$	$4.7K\Omega$	$4.538K\Omega$	-3.4468%
$R_4$	$2.2K\Omega$	$2.165K\Omega$	-1.5909%
$R_5$	$1.0K\Omega$	$0.980K\Omega$	-2.0000%
$R_{eq1}$	$3.2K\Omega$	$3.148K\Omega$	-1.625 %
$R_{eq2}$	$1.2073K\Omega$	$1.194K\Omega$	-1.1016 %
$R_{eq}$	$2.7073K\Omega$	$2.695K\Omega$	-0.4543%
$V_S$	8 [V]	8.035 [V]	-0.4375%
$V_1$	4.432 [V]	4.408 [V]	-0.5415%
$V_2$	3.555 [V]	3.606 [V]	1.4346%
$V_3$	3.553 [V]	3.575 [V]	0.6192%
$V_4$	2.444 [V]	2.433 [V]	-0.4501%
$V_5$	1.111 [V]	1.111 [V]	0%
$V_A$	8 [V]	8.032 [V]	0.4000%
$V_B$	3.567 [V]	3.612 [V]	1.2615%
$V_C$	1.123 [V]	1.140 [V]	1.5138%
$I_1$	2.954 [mA]	2.973 [mA]	0.6432%
$I_2$	1.0774 [mA]	1.085 [mA]	0.7054%
$I_3$	0.756 [mA]	0.770 [mA]	1.8519%
$I_4$	1.111 [mA]	1.111 [mA]	0%

# 2

$$V_1 = I_1 * R_1 = 2.973[mA] * 1.475[K\Omega] = 4.3851[V]$$

$$V_2 = I_2 * R_2 = 1.0774[mA] * 3.345[K\Omega] = 3.6039[V]$$

$$V_3 = I_3 * R_3 = 0.770[mA] * 4.538[K\Omega] = 3.4942[V]$$

$$V_4 = I_4 * R_4 = 1.111[mA] * 2.165[K\Omega] = 2.4053[V]$$

$$V_5 = I_4 * R_5 = 1.111[mA] * 0.980[K\Omega] = 1.0888[V]$$

# 3

All of the measurements were within the error range of  $\pm 10\%$ . The greatest resistor error was resistor number three which had an error of  $-3.4468\%$ . The greatest voltage error was the voltage at node C with an error of  $1.5138\%$ . The most likely reason is that it is the farthest from the voltage supply, so the error in the resistor would combine resulting in a greater error. Current number three was the greatest off, however it was a minute value being measured. A reason for resistor degradation is overheating and crystalline break down. Resistors are also susceptible to temperature drift.